

YEAR 2016 SET 1

Q1 The man who is now Municipal Commissioner worked as _____
 (A) the security guard at a university
 (B) a security guard at the university
 (C) a security guard at university
 (D) the security guard at the university

S1 Correct option is (B).
 Option (A) and (D) cannot be the answers because of the word 'the security'

Q2 Nobody knows how the Indian cricket team is going to cope with the difficult and seamer-friendly wickets in Australia.
 Choose the option which is closest in meaning to the underlined phrase in the above sentence.
 (A) put up with (B) put in with
 (C) put down to (D) put up against


S1 Correct option is (A).
 'cope with' means put up with

Q3 Find the odd one in the following group of words.
 mock, deride, praise, jeer
 (A) mock (B) deride
 (C) praise (D) jeer

S1 Correct option is (C).
 mock, deride and jeer' are synonyms which means mockery. Therefore, the odd one is 'praise'

Q4 Pick the odd one from the following options.
 (A) CADBE (B) JHKIL
 (C) XWVYZ (D) ONPMQ

S1 Correct option is (D).

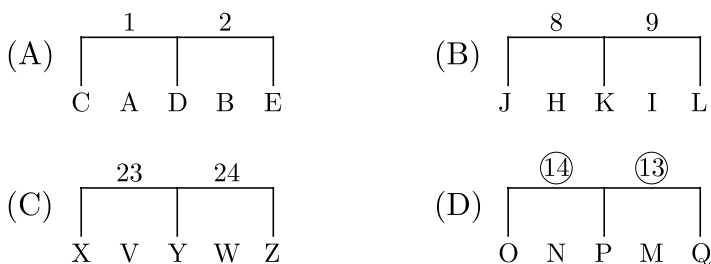

In options (A), (B) and (C), the letters skipped between consecutive pair of letters in the English alphabet is in increasing order (i.e) A and B, H and I and V and W but in option (D) N and M are present instead of M and N so, option (D) is odd one from the group.

Q5 In a quadratic function, the value of the product of the roots (α, β) is 4. Find the value of $\frac{\alpha^n + \beta^n}{\alpha^{-n} + \beta^{-n}}$
 (A) n^4 (B) 4^n
 (C) 2^{2n-1} (D) 4^{n-1}

S1 Correct option is (B).

$$\frac{\alpha^n + \beta^n}{\alpha^{-n} + \beta^{-n}} = \frac{\alpha^n + \beta^n}{\frac{1}{\alpha^n} + \frac{1}{\beta^n}}$$

$$= \frac{\alpha^n + \beta^n}{\frac{\beta^n + \alpha^n}{\alpha^n \beta^n}}$$

$$= \alpha^n \beta^n = (\alpha \beta)^n = (4)^n$$

Q.No 6-Q.No10 Carry two marks each

Q6 Among 150 faculty members in an institute, 55 are connected with each other through Facebook® and 85 are connected through WhatsApp®. 30 faculty members do not have Facebook® or WhatsApp® accounts. The number of faculty members connected only through Facebook® accounts is _____
 (A) 35 (B) 45
 (C) 65 (D) 90

S1 Correct option is (A).
 Total faculty members = 150
 The faculty members having facebook account = FB = 55
 The faculty members having whatsapp = W = 85
 The faculty members do not have face book (or) Whats App accounts = 30
 The faculty members having any account = 150 - 30 = 120
 The faculty members having both the accounts

$$= (FB + W) - 120$$


$$= (55 + 85) - 120$$

$$= 20$$

The number of faculty members connected only through Facebook accounts

$$= 55 - 20$$

$$= 35$$

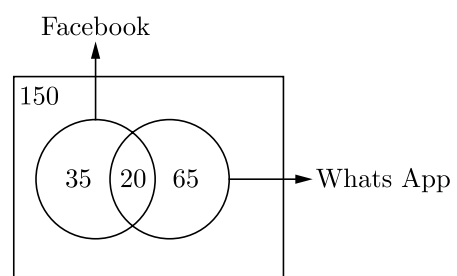

S1 Correct answer is 0.

$$\begin{aligned}
 f(x) &= x(x-1)(x-2) \text{ in } [1, 2] \\
 f'(x) &= 3x^2 - 6x + 2 \\
 &= 0 \\
 x &= \frac{3 \pm \sqrt{3}}{3} \\
 f''(x) &= 6x - 6 \\
 f''\left(\frac{3 + \sqrt{3}}{3}\right) &= 3.4 > 0 \Rightarrow \text{minimum} \\
 f''\left(\frac{3 - \sqrt{3}}{3}\right) &= -3.4 < 0 \Rightarrow \text{maximum} \\
 f(1) &= 0, f(2) = 0 \\
 \text{Max value} &= 0
 \end{aligned}$$

Q12 Consider 3×3 matrix with every element being equal to 1. Its only non-zero eigen value is _____

S1 Correct answer is 3.

$$A = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix}$$

Char equation is

$$\begin{aligned}
 |A - \lambda I| &= 0 \\
 -\lambda^3 + 3\lambda^2 &= 0 \\
 \lambda &= 3, 0, 0
 \end{aligned}$$

Q13 The Laplace Transform of $f(t) = e^{2t} \sin(5t) u(t)$ is

- (A) $\frac{5}{s^2 - 4s + 29}$ (B) $\frac{5}{s^2 + 5}$
 (C) $\frac{s-2}{s^2 - 4s + 29}$ (D) $\frac{5}{s+5}$

S1 Correct option is (A).

$$\begin{aligned}
 \sin 5t U(t) &\xrightarrow{LT} \frac{5}{s^2 + 5^2} \\
 e^{2t} \sin 5t U(t) &\xrightarrow{LT} \frac{5}{(s-2)^2 + 25} \\
 &\quad (\because e^{at} f(t) \xrightarrow{LT} F(s-a)) \\
 &= \frac{5}{s^2 + 4 - 2 \times 2(s) + 25} \\
 &= \frac{5}{s^2 + 4 - 4s + 25} \\
 &= \frac{5}{s^2 - 4s + 29} \\
 \therefore e^{2t} \sin 5t U(t) &\xrightarrow{LT} \frac{5}{s^2 - 4s + 29}
 \end{aligned}$$

Q14 A function $y(t)$, such that $y(0) = 1$ and $y(1) = 3e^{-1}$, is a solution of the differential equation $\frac{d^2 y}{dt^2} + 2\frac{dy}{dt} + y = 0$. Then $y(2)$ is

- (A) $5e^{-1}$ (B) $5e^{-2}$
 (C) $7e^{-1}$ (D) $7e^{-2}$

S1 Correct option is (B).

Given equation

$$\begin{aligned}
 m^2 + 2m + 1 &= 0 \\
 (m + 1)^2 &= 0
 \end{aligned}$$

Given $y(t) = (c_1 + c_2 t) e^{-t}$
 $y(0) = 1$
 $1 = c_1$
 Given $y(1) = 3e^{-1}$
 $3e^{-1} = (1 + c_2) e^{-1}$
 $3 = 1 + c_2$
 $c_2 = 2$
 $\therefore y(t) = (1 + 2t) e^{-t}$
 $y(2) = 5e^{-2}$

Q15 The value of the integral $\oint_C \frac{2z+5}{\left(z-\frac{1}{2}\right)(z^2-4z+5)} dz$

over the contour $|z|=1$, taken in the anti-clockwise direction, would be

- (A) $\frac{24\pi i}{13}$ (B) $\frac{48\pi i}{13}$
 (C) $\frac{24}{13}$ (D) $\frac{12}{13}$

S1 Correct option is (B).

$$\begin{aligned}
 f(z) &= \frac{2\left(\frac{1}{2}\right) + 5}{\left(\frac{1}{2}\right)^2 - 4\left(\frac{1}{2}\right) + 5} \\
 &= \frac{6}{\frac{1}{4} - 2 + 5} \\
 &= \frac{6}{\frac{13}{4}} = \frac{24}{13}
 \end{aligned}$$

$$\begin{aligned}
 \text{Ans} &= 2\pi i [\text{sum of residues}] \\
 &= 2\pi i \times \frac{24}{13} = \frac{48\pi i}{13}
 \end{aligned}$$

Q16 The transfer function of a system is $\frac{Y(s)}{R(s)} = \frac{s}{s+2}$.

The steady state output $y(t)$ is $A \cos(2t + \phi)$ for the input $\cos(2t)$. The values of A and ϕ , respectively are

- (A) $\frac{1}{\sqrt{2}}, -45^\circ$ (B) $\frac{1}{\sqrt{2}}, +45^\circ$
 (C) $\sqrt{2}, -45^\circ$ (D) $\sqrt{2}, +45^\circ$

S1 Correct option is (B).

$$\begin{aligned}
 A &= \left| \frac{j\omega}{j\omega + 2} \right|_{\omega=2} \\
 &= \frac{2}{\sqrt{2^2 + 2^2}} = \frac{2}{2\sqrt{2}} = \frac{1}{\sqrt{2}} \\
 \phi &= \angle \frac{j\omega}{j\omega + 2} \Big|_{\omega=2} \\
 &= 90^\circ - \tan^{-1} \frac{2}{2} = 45^\circ
 \end{aligned}$$

Q17 The phase cross-over frequency of the transfer function $G(s) = \frac{100}{(s+1)^3}$ in rad/s is

- (A) $\sqrt{3}$ (B) $\frac{1}{\sqrt{3}}$
 (C) 3 (D) $3\sqrt{3}$

S1 Correct option is (A).

$$\angle \frac{100}{(j\omega + 1)^3} = -180^\circ \Big|_{\omega=\omega_{pc}}$$

$$-3 \tan^{-1} \omega_{pc} = -180$$

$$\omega_{pc} = \sqrt{3}$$

- Q18** Consider a continuous-time system with input $x(t)$ and output $y(t)$ given by $y(t) = x(t) \cos(t)$. This system is
- (A) linear and time-invariant
 - (B) non-linear and time-invariant
 - (C) linear and time-varying
 - (D) non-linear and time-varying

S1 Correct option is (C).
 given $y(t) = x(t) \cos(t)$
 It satisfies both additivity and Homogeneity principles, so it is linear

It the input is delayed by t_0
 $y_1(t) = x(t - t_0) \cos(t)$

If the output is delayed by t_0
 $y(t - t_0) = x(t - t_0) \cos(t - t_0)$
 $= x(t - t_0) \cos(t - t_0)$

here, $y_1(t) \neq y(t - t_0)$, So, it is time varying.

Q19 The value of $\int_{-\infty}^{+\infty} e^{-t} \delta(2t - 2) dt$, where $\delta(t)$ is the Dirac delta function is

- (A) $\frac{1}{2e}$
- (B) $\frac{2}{e}$
- (C) $\frac{1}{e^2}$
- (D) $\frac{1}{2e^2}$

S1 Correct option is (A).

$$\int_{-\infty}^{+\infty} e^{-t} \delta(2t - 2) dt = \int_{-\infty}^{\infty} e^{-t} \delta(2(t - 1)) dt$$

$$= \int_{-\infty}^{\infty} e^{-t} \frac{1}{2} \delta(t - 1) dt$$

$$= \frac{1}{2} \int_{-\infty}^{\infty} e^{-t} \delta(t - 1) dt$$

$$= \frac{1}{2} e^{-1} = \frac{1}{2e}$$

Q20 A temperature in the range of -40°C to 55°C is to be measured with a resolution of 0.1°C . The minimum number of ADC bits required to get a matching dynamic range of the temperature sensor is

- (A) 8
- (B) 10
- (C) 12
- (D) 14

S1 Correct option is (B).

$$\frac{55 - (-40)}{2^n} \leq 0.1$$

$$\frac{95}{2^n} \leq 0.1$$


$$950 \leq 2^n$$

The minimum n value which can satisfy the above equation is 10

\therefore The minimum number of bits are 10.

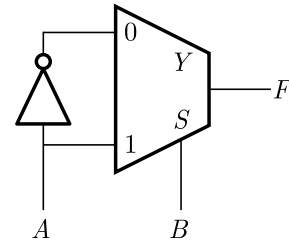Q21 Consider the following circuit which uses a 2-to-1

multiplexer as shown in the figure below. The Boolean expression for output F in terms of A and B is



- (A) $A \oplus B$
- (B) $\overline{A + B}$
- (C) $A + B$
- (D) $\overline{A \oplus B}$

S1 Correct option is (D).


$$F = \overline{S}I_0 + SI_1$$

$$= \overline{B} \overline{A} + BA$$


$$= A \odot B$$

$$= \overline{A \oplus B}$$

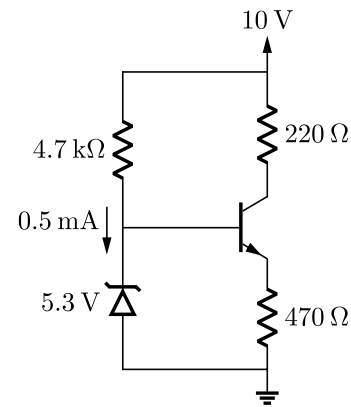Q22 A transistor circuit is given below. The Zener diode breakdown voltage is 5.3 V as shown. Take base to emitter voltage drop to be 0.6 V. The value of the current gain β is _____.



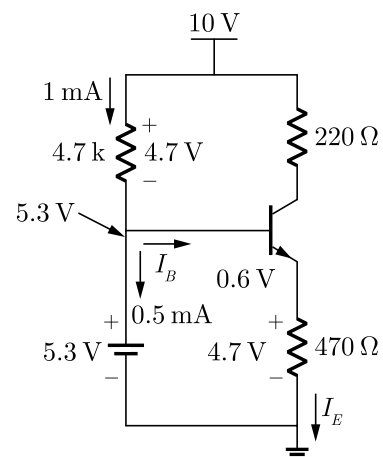S1 Correct answer is 19.
 Zener diode is in breakdown, replace it with a voltage source of value $V_Z = 5.3\text{ V}$ and $V_{BE} = 0.6\text{ V}$



Applying KCL at Base, we get

$$I_B = 1 - 0.5 = 0.5\text{ mA}$$

$$I_E = \frac{4.7}{470} = 10\text{ mA}$$

$$I_E = (\beta + 1) I_B$$

$$\beta + 1 = \frac{I_E}{I_B} = \frac{10}{0.5} = 20$$

$\beta = 19$

Q23 In cylindrical coordinate system, the potential produced by a uniform ring charge is given by $\phi = f(r, z)$, where f is a continuous function of r and z . Let \vec{E} be the resulting electric field. Then the magnitude of $\nabla \times \vec{E}$

- (A) Increase with r
- (B) is 0
- (C) is 3
- (D) decrease with z


S1 Correct option is (B).

A uniformly charged ring is specified. It can be considered as static. A static electric charge produces an electric field for which $\nabla \times \vec{E} = 0$.

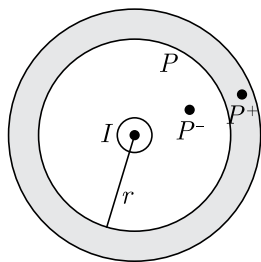Q24 A soft-iron toroid is concentric with a long straight conductor carrying a direct current I . If the relative permeability μ_r of soft-iron is 100, the ratio of the magnetic flux densities at two adjacent points located just inside and just outside the toroid is _____.

S1 Correct answer is 100.

A 2-dimensional view of a toroidal core is shown. Problem does not give any coil wound around the toroid.




$\vec{B}(P^-)$ due to straight conductor $= \frac{\mu_o I}{2\pi r} T$

$\vec{B}(P^+)$ due to straight conductor $= \frac{100\mu_o I}{2\pi r} T$


$\frac{\vec{B}(P^+)}{\vec{B}(P^-)} = 100$

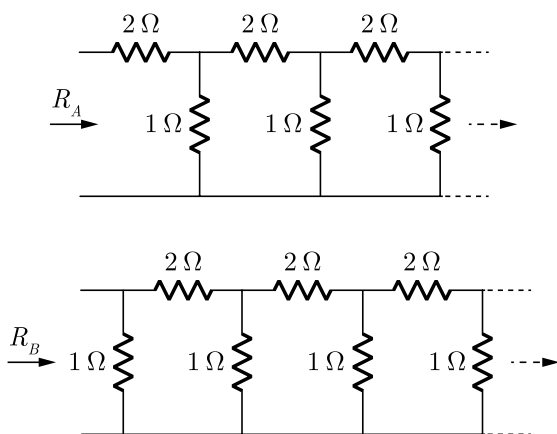Q25 R_A and R_B are the input resistances of circuits as shown below. The circuits extend infinitely in the direction shown. Which one of the statements is TRUE?



- (A) $R_A = R_B$
- (B) $R_A = R_B = 0$
- (C) $R_A < R_B$
- (D) $R_B = \frac{R_A}{(1 + R_A)}$

S1 Correct option is (D).

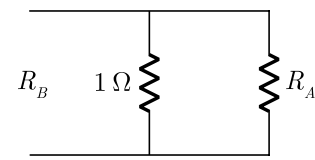

$R_B = \frac{1 \times R_A}{1 + R_A}$

Q26 In a constant V/f induction motor drive, the slip at the maximum torque

- (A) is directly proportional to the synchronous speed.
- (B) remains constant with respect to the synchronous speed.
- (C) has an inverse relation with the synchronous speed.
- (D) has no relation with the synchronous speed.


S1 Correct option is (C).

In an induction motor operating at any voltage V_r , frequency f , slip for max torque


$= \frac{r_2}{x_2}$ where $x_2 = 2\pi L_2 f$.

Now; if frequency is changed (irrespective of whether v/f is constant or not) x_2 changes proportionally. So slip for maximum torque is inversely proportional to frequency. Synchronous speed is directly proportional to frequency. Hence slip of maximum torque has an inverse relation with synchronous speed.

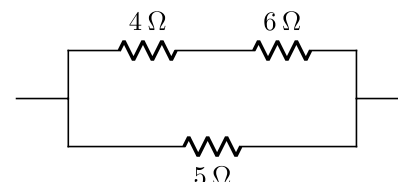Q27 In the portion of a circuit shown, if the heat generated in 5Ω resistance is 10 calories per second then heat generated by the 4Ω resistance, in calories per second, is _____.




S1 Correct answer is 2.

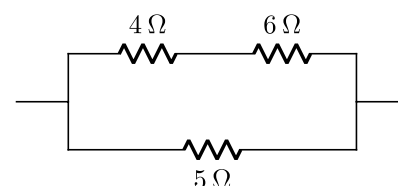

Heat generated by 5Ω is 10 calories per sec
1 calorie per second = 4.184 W

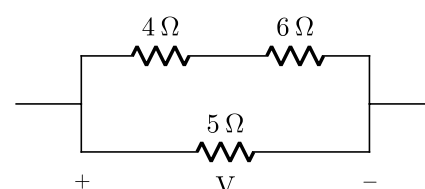So, power dissipated in 5Ω is $4.184 \times 10 = 41.84$ W



So, $\frac{V^2}{5} = 41.84$

$$V = \sqrt{5(41.84)}$$


$$V = 14.4637$$

So, Voltage across 4Ω is $= 14.4637 \left[\frac{4}{10} \right]$
 $= 5.78548 \text{ V}$


$$P_{4\Omega} = \frac{(5.78548)^2}{4} = 8.3679 \text{ Watt}$$

$$= 2 \text{ calories per second}$$

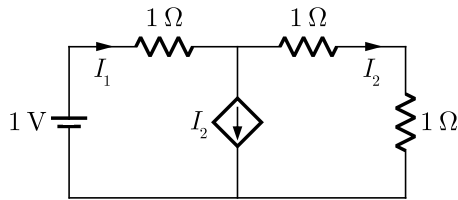Q28 In the given circuit, the current supplied by the battery, in ampere, is _____



S1 Correct answer is 0.5.

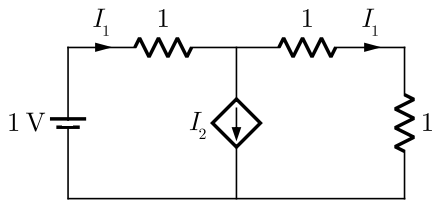

KVL $-1 + I_1 + 2I_2 = 0$
 $I_1 + 2I_2 = 1$... (1)

Also $I_1 = 2I_2$... (2)

So, current through battery means $I_1 = \frac{1}{2} \text{ A}$

Q29 In a 100 bus power system, there are 10 generators. In a particular iteration of Newton Raphson load flow technique (in polar coordinates), two of the PV buses are converted to PQ type. In this iteration

- (A) the number of unknown voltage angles increases by two and the number of unknown voltage magnitudes increases by two
- (B) the number of unknown voltage angles remains unchanged and the number of unknown voltage magnitudes increases by two
- (C) the number of unknown voltage angles increases by two and the number of unknown voltage magnitudes decreases by two
- (D) the number of unknown voltage angles remains unchanged and the number of unknown voltage magnitudes decreases by two

S1 Correct option is (B).

Total No. of buses = 100
 Generator bus = $10 - 1 = 9$
 Load busses = 90
 Slack bus = 1

If 2 buses are converted to PQ from PV it will add 2 unknown voltages to iteration but unknown angles remain constant.

Q30 The magnitude of three-phase fault currents at buses A and B power system are 10 pu and 8 pu, respectively. Neglect all resistances in the system and consider the pre-fault system to be unloaded. The pre-fault voltage at all buses in the system is 1.0 pu. The voltage magnitude at bus B during a three-phase fault at bus A is 0.8 pu. The voltage magnitude at bus A during a three-phase fault at bus B in pu, is _____.

S1 Correct answer is 0.84.

Post fault voltage at bus B for fault at bus A is

$$V_{BAF} = V_{BBF} - Z_{AB} I_{FA} = 0.8$$

$$1 - Z_{AB} \cdot 10 = 0.8$$

$$Z_{AB} = 0.02$$

Post fault voltage at bus A for fault at Bus B

$$V_{AAF} = V_{ABF} - Z_{AB} I_{FB}$$

$$= 1 - 0.02 \times 8$$

$$= 1 - 0.16$$

$$= 0.84 \text{ pu}$$

Q31 Consider a system consisting of a synchronous generator working at a lagging power factor, a synchronous motor working at an overexcited condition and a directly grid-connected induction generator. Consider capacitive VAR to be a source and inductive VAR to be a sink of reactive power


Which one of the following statements is TRUE?

- (A) Synchronous motor and synchronous generator are sources and induction generator is a sink of reactive power.
- (B) Synchronous motor and induction generator are sources and synchronous generator is a sink of reactive power.
- (C) Synchronous motor is a source and induction generator and synchronous generator are sinks of reactive power.
- (D) All the sources of reactive power.


S1 Correct option is (A).

Sync. Generator with lagging PF \Rightarrow supply P & Q
 Sync. Motor with over excitation \Rightarrow supply Q
 Induction motor \Rightarrow Absorbs Q

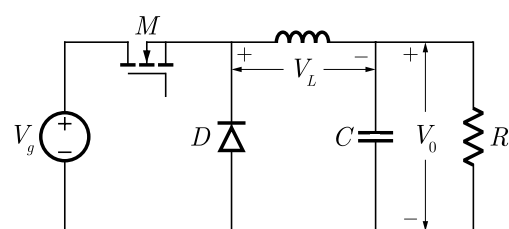Q32 A buck converter, as shown in Figure (a) below, is working in steady state. The output voltage and the inductor current can be assumed to be ripple free. Figure (b) shows the inductor voltage V_L during a complete switching interval. Assuming all devices are ideal, the duty cycle of the buck converter is _____.



(a)

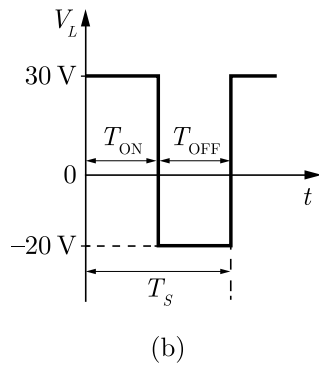

S1 Correct answer is 0.4.

In steady state, area of inductor voltage for one switching cycle is zero

$$30 \times T_{ON} - 20 \times T_{OFF} = 0$$

$$\frac{T_{ON}}{T_{OFF}} = \frac{2}{3}$$



Duty cycle

$$D = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$


$$= \frac{T_{ON}}{T_{ON} + \frac{3}{2}T_{ON}}$$

$$= \frac{2}{5} = 0.4$$

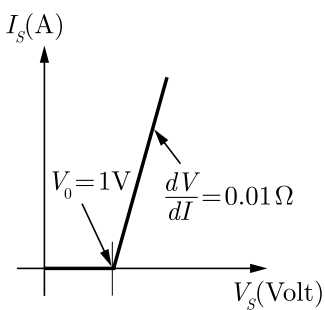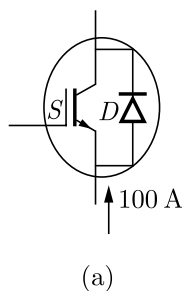Q33 A steady dc current of 100 A is flowing through a power module (S, D) as shown in Figure (a). The V-I characteristics of the IGBT (S) and the diode (D) are shown in Figure (b) and (c), respectively. The conduction power loss in the power module (S, D) in watts, is _____



V-I characteristic of IGBT
(b)

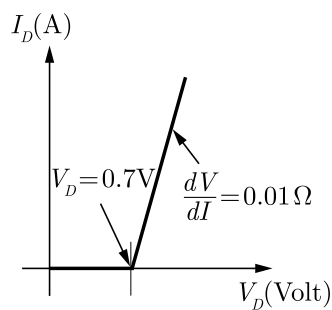

V-I characteristic of diode
(c)

S1 Correct answer is 170.


No current flows through the IGBT. So current flows only in Diode

$$\text{Conduction loss} = V_t I_{av} + I_{rms}^2 R_{on}$$

$$= 0.7 \times 100 + 100^2 \times 0.01$$

$$= 170 \text{ W}$$

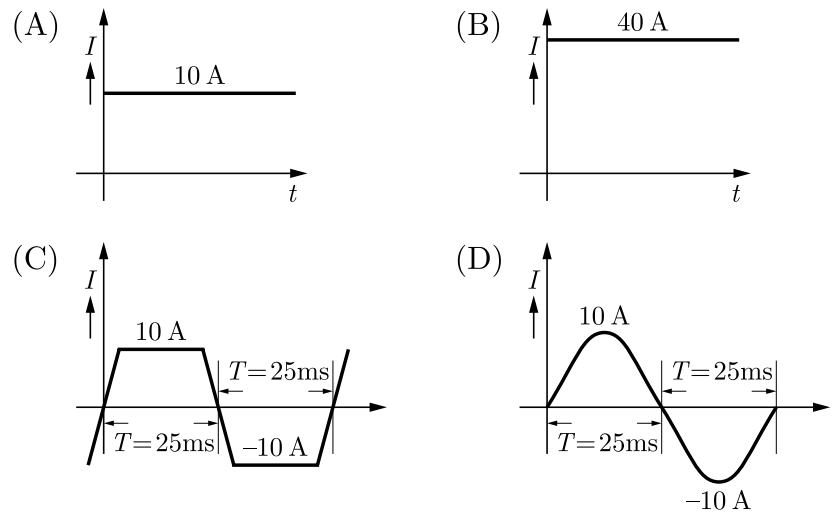Q34 A 4-pole, lap-connected separately excited dc motor is drawing a steady current of 40 A while running at 600 rpm. A good approximation for the waveshape of the current in an armature conductor of the motor is given by




S1 Correct option is (C).

With lap winding, and 4 poles, number of parallel paths = 4, with a total armature current of 40 A; current in each path and hence current in each armature conductor is 10 A. It remains constant at 10 A as long as the conductor is in one path. When it goes into the next path (due to commutator action) the current in it reverses and becomes 10 A. Assuming straight line commutation, the change from (+10 A) to (-10 A) is linear.

With 600 RPM; time for 1 revolution = 0.1 sec. Time of a conductor to cover 1 pole-pitch = $0.1/4 = 25 \text{ ms}$. This is the width of one half cycle of conductor current.

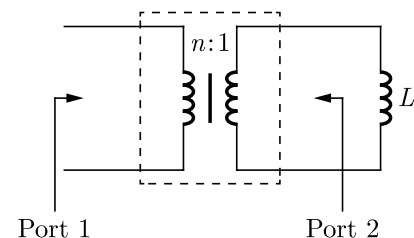Q35 If an ideal transformer has an inductive load element at port 2 as shown in the figure below, the equivalent inductance at port 1 is



- (A) nL
- (B) n^2L
- (C) $\frac{n}{L}$
- (D) $\frac{n^2}{L}$

S1 Correct option is (B).

An inductance of LH in the low voltage side becomes $n^2 LH$ referred to the high voltage side (hv turns/lv turns = n)

Q.No 36-65 Carry Two marks each

Q36 Candidates were asked to come to an interview with 3 pens each. Black, blue, green and red were the permitted pen colours that the candidate could bring.

The probability that a candidate comes with all 3 pens having the same colour is _____.

S1 Correct answer is 0.2.

$$\begin{aligned} \text{Total no. of cases} &= 4C_1 + 4C_2 + 4C_2 + 4C_3 \\ &= 20 \end{aligned}$$

$$\text{Favorable cases} = 4C_1 = 4$$

$$\therefore \text{Required probability} = \frac{4}{20} = 0.2$$

Q37 Let $S = \sum_{n=0}^{\infty} n\alpha^n$ where $|\alpha| < 1$. The value of α in the range $0 < \alpha < 1$, such that $S = 2\alpha$ is _____

S1 Correct answer is 0.2928.

Given
$$S = \sum_{n=0}^{\infty} n\alpha^n$$

$$S = 0 + 1\alpha + 2\alpha^2 + 3\alpha^3 + \dots \infty$$

$$S = \alpha + 2\alpha^2 + 3\alpha^3 + \dots \infty$$

$$S = \frac{\alpha}{(1-\alpha)^2} \quad (\because 0 < \alpha < 1)$$

but gives, $S = 2\alpha$

$$\frac{\alpha}{(1-\alpha)^2} = 2\alpha$$

$$\frac{1}{2} = (1-\alpha)^2$$

$$(1-\alpha) = \pm \frac{1}{\sqrt{2}}$$

$$1-\alpha = \frac{1}{\sqrt{2}} \text{ or } 1-\alpha = -\frac{1}{\sqrt{2}}$$

$$1 - \frac{1}{\sqrt{2}} = \alpha \text{ or } 1 + \frac{1}{\sqrt{2}} = \alpha$$

$$\alpha = 1 - 0.707 \text{ or } \alpha = 1.707$$

$$\alpha = 0.2928$$

But given that $0 < \alpha < 1$,

So, $\alpha = 0.2928$

Q38 Let the Eigen values of a 2×2 matrix A be 1, -2 with eigenvectors x_1 and x_2 respectively. Then the Eigen values and eigenvectors of the matrix $A^2 - 3A + 4I$ would respectively, be

(A) 2, 14; x_1, x_2 (B) 2, 14; $x_1 + x_2, x_1 - x_2$

(C) 2, 0; x_1, x_2 (D) 2, 0; $x_1 + x_2, x_1 - x_2$

S1 Correct option is (A).

$$A \rightarrow 1, -2$$

$$A^2 \rightarrow 1, 4$$

$$-3A \rightarrow -3, 6$$

$$4I \rightarrow 4, 4$$

$$A^2 - 3A + 4I \rightarrow 2, 14$$

\therefore eigen values 2, 14

Eigen vectors do not change.

Q39 Let A be a 4×3 real matrix which rank 2. Which one of the following statement is TRUE?

(A) Rank of A^T is less than 2

(B) Rank of $A^T A$ is equal to 2

(C) Rank of $A^T A$ is greater than 2

(D) Rank of $A^T A$ can be any number between 1 and 3

S1 Correct option is (B).


$$\rho(A_{4 \times 3}) = 2; \rho(A_{3 \times 4}^T) = 2$$

$$\rho(A \times B) \leq \min[\rho(A), \rho(B)]$$

AA^T of order 4×4 whose rank ≤ 2

$A^T A$ is of order 3×3 whose rank ≤ 2

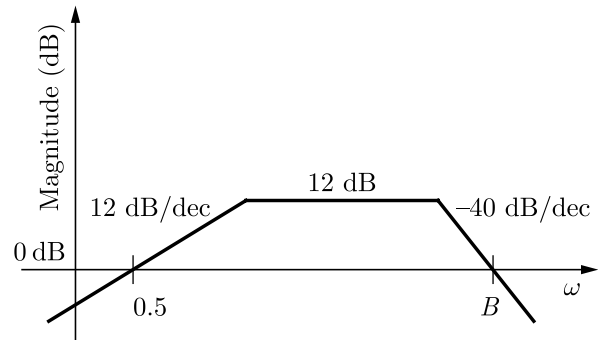Q40 Consider the following asymptotic Bode magnitude plot (ω is in rad/s)



Which one of the following transfer functions is best represented by the above Bode magnitude plot?

(A) $\frac{2s}{(1+0.5s)(1+0.25s)^2}$ (B) $\frac{4(1+0.5s)}{s(1+0.25s)}$

(C) $\frac{2s}{(1+2s)(1+4s)}$ (D) $\frac{4s}{(1+2s)(1+4s)^2}$

S1 Correct option is (A).

From the given Bode plot the corner frequencies are 2 rad/sec and 4 rad/sec

$$TF = \frac{Ks}{\left(1 + \frac{s}{2}\right)\left(1 + \frac{s}{4}\right)^2}$$

$$20 \log K + 20 \log \omega = 0 \text{ dB at } \omega = 0.5$$

$$K = 2$$

$$\therefore TF = \frac{2s}{(1+0.5s)(1+0.25s)^2}$$

Q41 Consider the following state - space representation of a linear time-invariant system.

$$\dot{x}(t) = \begin{bmatrix} 1 & 0 \\ 0 & 2 \end{bmatrix} x(t), y(t) = c^T x(t), c = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \text{ and } x(0) = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

The value of $y(t)$ for $t = \log_e 2$ is _____

S1 Correct answer is 6.

$$y(t) = c^T x(t)$$

$$x(t) = e^{At} x(0)$$

$$e^{At} = L^{-1}[(SI - A)^{-1}]$$

$$SI - A = \begin{bmatrix} s-1 & 0 \\ 0 & s-2 \end{bmatrix}$$

$$(SI - A)^{-1} = \begin{bmatrix} \frac{1}{s-1} & 0 \\ 0 & \frac{1}{s-2} \end{bmatrix}$$

$$e^{At} = \begin{bmatrix} e^t & 0 \\ 0 & e^{2t} \end{bmatrix}$$


$$x(t) = \begin{bmatrix} e^t & 0 \\ 0 & e^{2t} \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} = \begin{bmatrix} e^t \\ e^{2t} \end{bmatrix}$$

$$y(t) = [1 \ 1] \begin{bmatrix} e^t \\ e^{2t} \end{bmatrix}$$

$$= [e^t + e^{2t}]_{t=0.693}, t = \ln_e(2) = 0.693$$

$$= [2 + 4] = 6$$

$$y(t) = 6$$

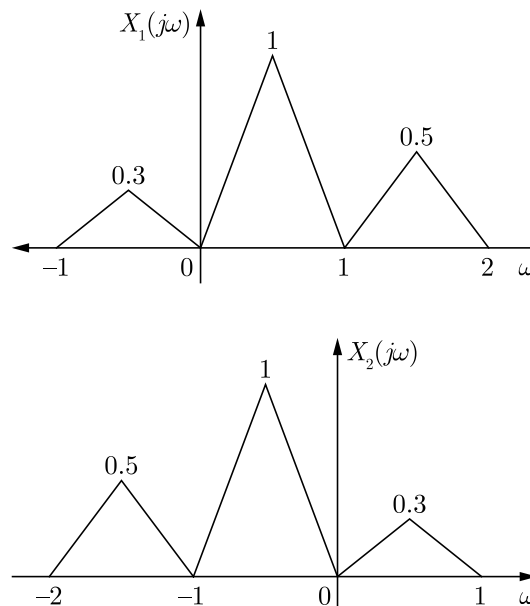

Q42 Loop transfer function of a feedback system is $G(s)H(s) = \frac{s+3}{s^2(s-3)}$. Take the Nyquist contour in the clockwise direction. Then the Nyquist plot of $G(s)$ encircles $-1 + j0$.

- (A) once in clockwise direction
- (B) twice in clockwise direction
- (C) once in anti clockwise direction
- (D) twice in anti clockwise direction

S1 Correct option is (A).

$$CE = 1 + \frac{s+3}{s^3-3s^2} = 0$$

$$s^3 - 3s^2 + s + 3 = 0$$

$$\begin{array}{l|ll} s^3 & 1 & 1 \\ s^2 & -3 & 3 \\ s^1 & 2 & \\ s^0 & 3 & \end{array}$$

Unstable with two right half of s-plane poles

$$\therefore Z = 2, P = 1$$

$$N = P - Z$$

$$N = 1 - 2 = -1 \text{ once in the cw direction}$$

Q43 Given the following polynomial equation $S^3 + 5.5S^2 + 8.5S + 3 = 0$ the number of roots of the polynomial which have real parts strictly less than -1 is

S1 Correct answer is 2.

$$(Z-1)^3 + (5.5)(Z-1)^2 + 8.5(Z-1) + 3 = 0$$

$$Z^3 - 3Z^2 + 3Z - 1 + 5.5Z^2 - 11Z + 5.5 + 8.5Z - 8.5 + 3 = 0$$

$$Z^3 + 2.5Z^2 + 0.5Z - 1 = 0$$

$$\begin{array}{l|ll} +Z^3 & 1 & 0.5 \\ +Z^2 & 2.5 & -1 \\ +Z^1 & 2.25 & \\ -Z^0 & -1 & \end{array}$$

Two roots real parts are less than -1

Q44 Suppose $x_1(t)$ and $x_2(t)$ have the Fourier transforms as shown below

Which one of the following statements is TRUE?

- (A) $x_1(t)$ and $x_2(t)$ are complex and $x_1(t)x_2(t)$ is also complex with nonzero imaginary part
- (B) $x_1(t)$ and $x_2(t)$ are real and $x_1(t)x_2(t)$ is also real
- (C) $x_1(t)$ and $x_2(t)$ are complex but $x_1(t)x_2(t)$ is real
- (D) $x_1(t)$ and $x_2(t)$ are imaginary but $x_1(t)x_2(t)$ is real

S1 Correct option is (C).

$$\text{Atri}\left(\frac{t}{T}\right) \longleftrightarrow ATsa^2\left(\frac{\omega T}{2}\right)$$

From duality properly

$$ATs_a^2\left(\frac{tT}{2}\right) \longleftrightarrow 2\pi \left[\text{Atri}\left(\frac{-\omega}{T}\right) \right]$$

$$TSa^2\left(\frac{tT}{2}\right) \longleftrightarrow 2\pi \text{tri}\left(\frac{\omega}{T}\right)$$

$$T = \frac{1}{2}$$

$$\frac{1}{2}Sa^2\left(\frac{tT}{2}\right) \longleftrightarrow 2\pi \text{tri}(2\omega)$$

$$\frac{1}{4\pi}sa^2\left(\frac{tT}{2}\right) \longleftrightarrow \text{tri}(2\omega)$$

Assume $x(t) = \frac{1}{4\pi}sa^2\left(\frac{tT}{2}\right)$

$$X(\omega) = \text{tri}(2\omega)$$

$x(t)$ is real function

$$X_1(\omega) = X\left(\omega - \frac{1}{2}\right) + \frac{1}{2}X\left(\omega - \frac{3}{2}\right) + 0.3X\left(\omega + \frac{1}{2}\right)$$

$$x_1(t) = e^{j\frac{1}{2}t}x(t) + \frac{1}{2}e^{j\frac{3}{2}t}x(t) + 0.3e^{-j\frac{1}{2}t}x(t)$$

$x_2(t)$ is complex function

$$X_2(\omega) = x_1(-\omega)$$

$$x_2(t) = x_1(-t)$$

$$x_2(t) = e^{-j\frac{1}{2}t}x(-t) + \frac{1}{2}e^{-j\frac{3}{2}t}x(-t) + 0.3e^{j\frac{1}{2}t}x(-t) = x(t)$$

$$x_2(t) = e^{-j\frac{1}{2}t}x(t) + \frac{1}{2}e^{-j\frac{3}{2}t}x(t) + 0.3e^{j\frac{1}{2}t}x(t)$$

$x_2(t)$ is complex function

$$x_1(t)x_2(t) = x^2(t) + \frac{1}{2}e^{-jt}x^2(t) + 0.3e^{jt}x^2(t) + \frac{1}{2}e^{jt}x^2(t)$$

$$+ \frac{1}{4}x^2(t) + 0.15e^{+j2t}x^2(t) + 0.3e^{-jt}x^2(t)$$

$$+ 0.15e^{-j2t}x^2(t) + 0.09x^2(t)$$

$$x_1(t)x_2(t) = x^2(t)[1.34 + \cos t + 0.6 \cos t$$


$$+ 0.3 \cos 2t] x_1(t)x_2(t) \text{ is real function}$$

Q45 The output of a continuous-time linear time-invariant system is denoted by $T\{x(t)\}$ where $x(t)$ is the input signal. A signal $z(t)$ is called eigen-signal of the system T , when $T\{z(t)\} = \gamma z(t)$, where γ is a complex number, in general and is called an eigenvalue of T . Suppose the impulse response of the system T is real and even. Which of the following statements is TRUE?

- (A) $\cos(t)$ is an eigen-signal but $\sin(t)$ is not
- (B) $\cos(t)$ and $\sin(t)$ are both eigen-signals but with different eigenvalues
- (C) $\sin(t)$ is an eigen-signal but $\cos(t)$ is not
- (D) $\cos(t)$ and $\sin(t)$ are both eigen-signals with identical eigenvalues

S1 Correct option is (D).

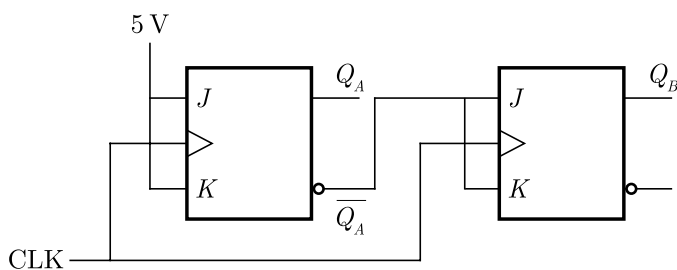Q46 The current state $Q_A Q_B$ of a two JK flip-flop system is 00. Assume that the clock rise-time is much smaller than the delay of the JK flip-flop. The next state of the system is




- (A) 00
- (B) 01
- (C) 11
- (D) 10

S1 Correct option is (C).

PS		PI		NS			
Q_A	Q_B	J_A	k_A	$J_B(\overline{Q_A})$	$k_B(\overline{Q_A})$	Q_A^+	Q_B^+
		1	1				
0	0	1	1	1	1	1	1

The next state of the system $Q_A Q_B = 11$

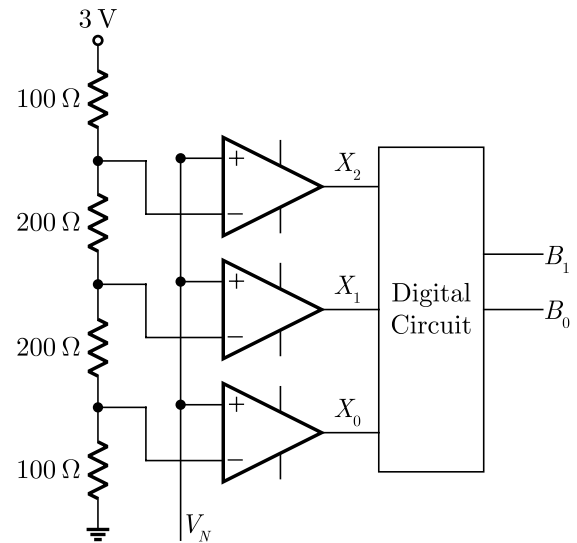Q47 A 2-bit flash Analog to Digital Converter (ADC) is given below. The input is $0 \leq V_N \leq 3$ Volts. The expression for the LSB of the output B_0 as a Boolean function of X_2 , X_1 and X_0 is



- (A) $X_0[\overline{X_2 \oplus X_1}]$
- (B) $\overline{X_0}[\overline{X_2 \oplus X_1}]$
- (C) $X_0[X_2 \oplus X_1]$
- (D) $\overline{X_0}[X_2 \oplus X_1]$

S1 Correct option is (A).

X_2	X_1	X_0	B_1	B_0
0	0	0	0	0
0	0	1	0	1
0	1	1	1	0
1	1	1	1	1

$$B_0 = \overline{X_2} \overline{X_1} X_0 + X_2 X_1 X_0$$


$$= [X_2 \overline{X_1} + X_2 X_1] X_0$$

$$(X_2 \odot X_1) X_0 = X_0 [\overline{X_2 \oplus X_1}]$$

Q48 Two electric charges q and $-2q$ are placed at $(0, 0)$ and $(6, 0)$ on the $x-y$ plane. The equation of the zero equipotential curve in the $x-y$ plane is

- (A) $x = -2$
- (B) $y = 2$
- (C) $x^2 + y^2 = 2$
- (D) $(x+2)^2 + y^2 = 16$

S1 Correct option is (D).

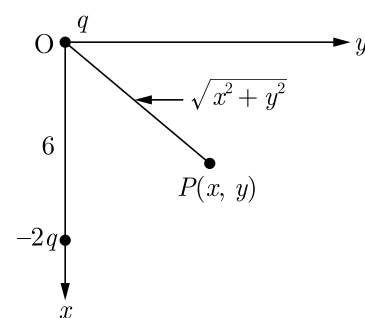

Potential at P due to q , at origin

$$= \frac{q}{4\pi\epsilon_0 \sqrt{x^2 + y^2}} V(\text{ref} : \infty)$$

Potential at P due to $-2q$ at $(6, 0)$

$$= \frac{-2q}{4\pi\epsilon_0 \sqrt{(x-6)^2 + y^2}} V$$


Net potential at (given)

$$P = \frac{q}{4\pi\epsilon_0} \left[\frac{1}{\sqrt{x^2 + y^2}} - \frac{2}{\sqrt{(x-6)^2 + y^2}} \right] = 0$$


$$\begin{aligned} \therefore 4(x^2 + y^2) &= (x - 6)^2 + y^2 \\ &= x^2 + 36 - 12x + y^2 \\ 3x^2 + 3y^2 &= 36 - 12x \\ x^2 + y^2 &= 12 - 4x \\ (x + 2)^2 + y^2 &= 16 \end{aligned}$$

(Equation of zero equipotential curve).

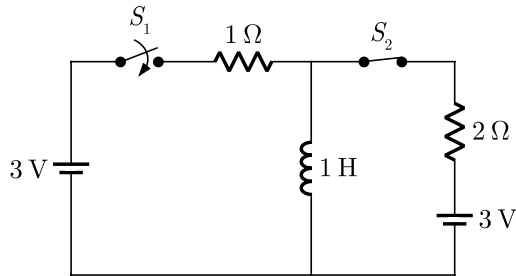
Q49 In the circuit shown, switch S_2 has been closed for a long time. At time $t = 0$ switch S_1 is closed. At $t = 0^+$, the rate of change of current through the inductor, in amperes per second, is _____



S1 Correct answer is 2.
 $t = 0^-$

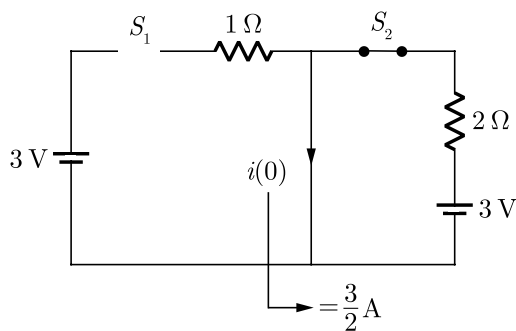

at $t = 0^+$

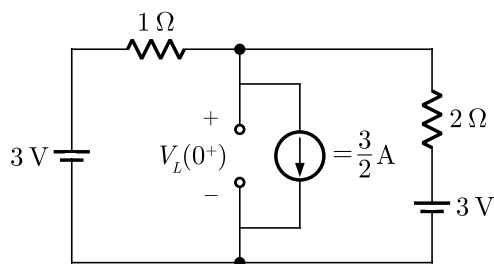

Nodal

$$\begin{aligned} \frac{(V_L(0^+) - 3)}{2} + \frac{3(V_L(0^+) - 3)}{2} &= 0 \\ \frac{2V_L(0^+) - 6 + 3V_L(0^+) - 9}{2} &= 0 \\ 3V_L(0^+) &= 6 \\ V_L(0^+) &= 2 \end{aligned}$$

So,

$$\begin{aligned} \frac{di(0^+)}{dt} &= \frac{V_L(0^+)}{L} \\ &= \frac{2}{1} = 2 \text{ A/sec} \end{aligned}$$

Q50 A three-phase cable is supplying 800 kW and 600 kVAr to an inductive load. It is intended to supply an additional resistive load of 100 kW through the same cable without increasing the heat dissipation in the cable, by providing a three-phase bank of capacitors connected in star across the load. Given the line voltage is 3.3 kV,

50 Hz the capacitance per phase of the bank expressed in microfarads, is _____

S1 Correct answer is 48.

Initial load = $(800 + j600)$

load after modification = $(900 + j600)$ to maintain same heat dissipation magnitude of power should be same

$$\begin{aligned} \text{Load with compensation} &= (900 + j600 \\ &\quad + \text{Compensation}) \\ &= (900 + jx) \end{aligned}$$

Equating magnitude of power

$$\begin{aligned} 800^2 + 600^2 &= 900^2 + x^2 \\ 8^2 + 6^2 &= 9^2 + x^2 \\ 100 &= 81 + x^2 \\ x &= \sqrt{19} = 4.3588 \end{aligned}$$

Require reactive power = 435.8 kVAr

After compensation

Reactive power to be compensated by capacitor to achieve this is 164.11 kVAr

$$\frac{V_{ph}^2}{X_C/\text{Phase}} = \frac{Q_C}{\text{Phase}}$$

$$\left(\frac{3.3k}{\sqrt{3}}\right)^2 \times \omega C_{ph} = \frac{164.11k}{3}$$

$$C_{ph} = 48 \mu\text{F}$$


Q51 A 30 MVA 3-phase, 50 Hz, 13.8 kV, star-connected synchronous generator has positive, negative and zero sequence reactances, 15%, 15% and 5% respectively. A reactance (X_n) is connected between the neutral of the generator and ground. A double line to ground fault takes place involving phases b and c , with a fault impedance of $j0.1$ p.u. The value of X_n (in p.u) that will limit the positive sequence current to 4270 A is

S1 Correct answer is 1.1.

Since all quantities are given in 'pu'

$$\begin{aligned} \text{Positive sequence current in pu} &= \frac{4270}{I_B} \\ &= \frac{4.27 \times \sqrt{3} \times 13.8}{30} \\ &= 3.4 \text{ pu} \end{aligned}$$

Equivalent circuit

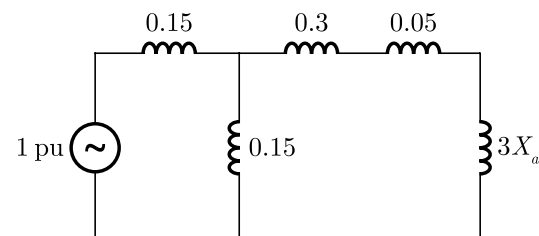

$$\text{Positive sequence current} = \frac{1}{X_{eq}} = 3.4$$

$$X_{eq} = \frac{1}{3.4} = 0.2941 \text{ pu}$$

$$0.15 + \frac{0.15(0.35 + 3X_n)}{3X_n + 0.5} = 0.2941$$


$$\frac{0.15(0.35 + 3X_n)}{3X_n + 0.5} = 0.1441$$

$$0.0525 + 0.45X_n = 0.4323X_n + 0.07205$$

$$0.0177X_n = 0.01955$$



$$X_n = 1.104 \text{ pu}$$

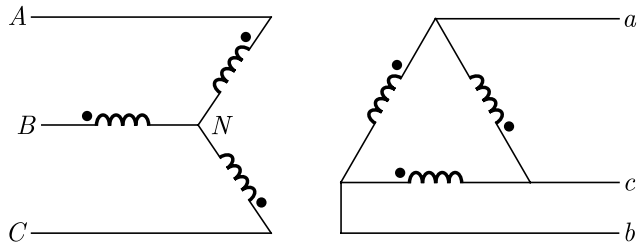Q52 If the star side of the star-delta transformer shown in the figure is excited by a negative sequence voltage, then



- (A) V_{AB} leads V_{ab} by 60°
- (B) V_{AB} lags V_{ab} by 60°
- (C) V_{AB} leads V_{ab} by 30°
- (D) V_{AB} lags V_{ab} by 30°

S1 Correct option is (D).

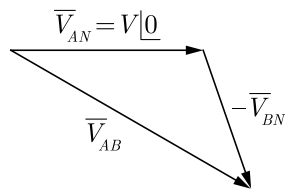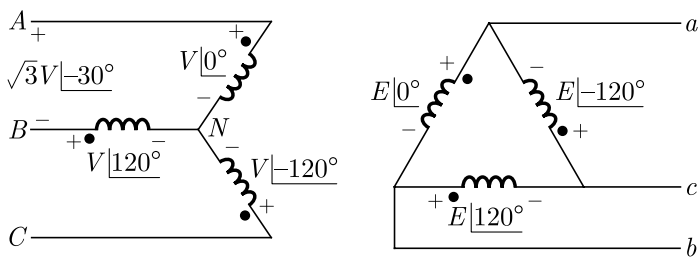

With -ve sequence voltage,

$$\bar{V}_{AN} = V \angle 0^\circ$$

$$\bar{V}_{BN} = V \angle 120^\circ$$

$$\bar{V}_{CN} = V \angle -120^\circ$$

$$\bar{V}_{AB} = \sqrt{3} V \angle -30^\circ$$

and

from figure

$$\bar{V}_{ab} = E \angle 0$$

$$\bar{V}_{AB} \text{ lags } \bar{V}_{ab} \text{ by } 30^\circ$$

Q53 A single-phase thyristor-bridge rectifier is fed from a 230 V, 50 Hz single-phase AC mains. If it is delivering a constant DC current of 10 A, at firing angle of 30° , then value of the power factor at AC mains is

- (A) 0.87
- (B) 0.9
- (C) 0.78
- (D) 0.45

S1 Correct option is (C).

Power factor at input mains


$$= \frac{2\sqrt{2}}{\pi} \cos \alpha$$

$$= 0.9 \times \cos 30^\circ$$


$$= 0.78$$

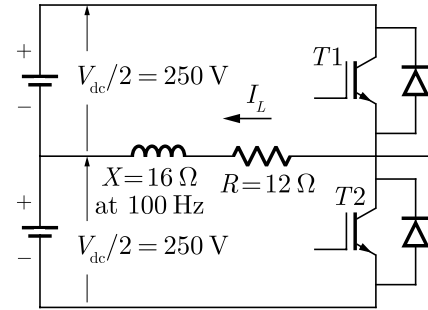Q54 The switches $T1$ and $T2$ in Figure are switched

in a complementary fashion with sinusoidal pulse width modulation technique. The modulating voltage $v_m(t) = 0.8 \sin(200\pi t)$ V and the triangular carrier (V_c), voltage (v_c) are as shown in figure (b). The carrier frequency is 5 kHz. The peak value of the 100 Hz component of the load current (i_L) in Ampere, is _____



(a)

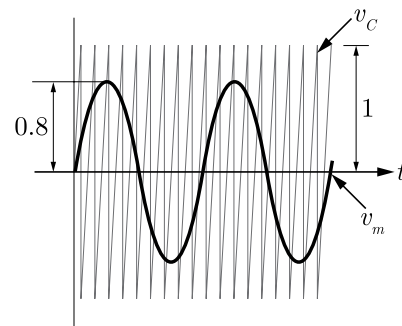

(b)

S1 Correct answer is 10.

Modulation index, $m_a = \frac{\hat{v}_m}{\hat{v}_{tri}} = \frac{0.8}{1} = 0.8$

Amplitude of the fundamental output voltage,

$$(\hat{V}_{AO})_1 = m_a \times \frac{V_{dc}}{2}$$

$$= 0.8 \times 250$$

$$= 200 \text{ V}$$

From the given modulating voltage equation, it can be understood that $\omega_1 = 200\pi$ means,

fundamental component frequency = 100 Hz

Load impedance at 100 Hz frequency,

$$Z_1 = \sqrt{R^2 + X^2}$$

$$= \sqrt{12^2 + 16^2}$$


$$= 20 \Omega$$

∴

$$\hat{I}_{L1} = \frac{\hat{V}_{AO1}}{Z_1}$$

$$= \frac{200}{20} = 10 \text{ A}$$

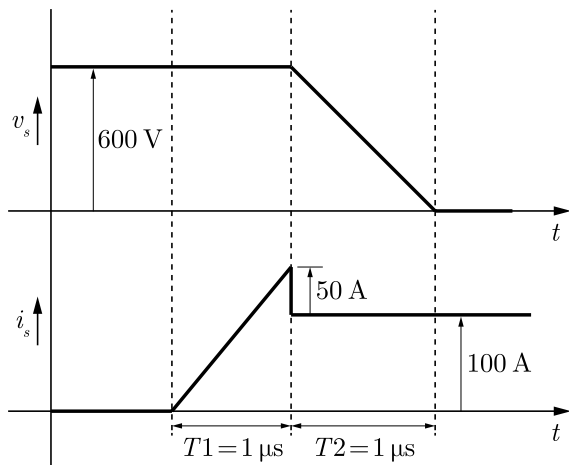Q55 The voltage (v_s) across the current (i_s) through a semiconductor switch during a turn-ON transition are shown in figure. The energy dissipated during the turn-ON transition, in mJ, is _____



S1 Correct answer is 75.

Energy loss during

$$\begin{aligned}
 T_1 &= \int_0^{T_1} v \cdot i dt = 600 \times \int_0^{T_1} i dt \\
 &= 600 \times \text{area under current curve} \\
 &= 600 \times \frac{1}{2} \times 150 \times 1 \times 10^{-6} \\
 &= 45 \text{ mJ}
 \end{aligned}$$

Energy loss during

$$\begin{aligned}
 T_2 &= \int_0^{T_2} v \cdot i dt = 100 \times \int_0^{T_2} v dt \\
 &= 100 \times \text{area under voltage curve} \\
 &= 100 \times \frac{1}{2} \times 600 \times 1 \times 10^{-6} \\
 &= 30 \text{ mJ}
 \end{aligned}$$

$$\begin{aligned}
 \text{Total energy loss} &= 45 + 30 \\
 &= 75 \text{ mJ}
 \end{aligned}$$

Q56 A single-phase 400 V, 50 Hz transformer has an iron loss of 5000 W at the rated condition. When operated at 200 V, 25 Hz, the iron loss is 2000 W. When operated at 416 V, 52 Hz the value of the hysteresis loss divided by the eddy current loss is _____

S1 Correct answer is 1.4423.

If v/f is kept constant, maximum core flux density is constant.

In the problem, $(400/50) = (200/25) = 8(416/52)$. v/f is kept constant. So the maximum core flux density is constant. Let it be B .

$$\begin{aligned}
 \text{Hysteresis loss} & \quad W_h = k_h f B^n \\
 \text{Eddy current loss} & \quad W_w = k_e f^2 B^2 \\
 \text{Total core loss} & = W_h + W_e
 \end{aligned}$$

At 400 V & 50 Hz,

$$\begin{aligned}
 k_h 50 B^n + k_e 50^2 B^2 &= 5000 \\
 \therefore k_h B^n + k_e 50 B^2 &= 100 \quad \dots(1)
 \end{aligned}$$

At 200 V, 25 Hz,

$$\begin{aligned}
 k_h 25 B^n + k_e 25^2 B^2 &= 2000 \\
 k_h B^n + k_e 25 B^2 &= 80 \quad \dots(2) \\
 k_e 25 B^2 &= 20; k_h B^n = 60
 \end{aligned}$$


At 416 V; 52 Hz;

$$\begin{aligned}
 (k_h B^n) 52 &= 60 \times 52 \\
 k_e 25^2 B^2 &= 0.8 \times 52^2 \\
 \frac{\text{Hysteresis loss}}{\text{Eddy current loss}} &= \frac{60 \times 52}{0.8 \times 52^2}
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{75}{52} \\
 &= 1.4423
 \end{aligned}$$

Q57 A DC shunt generator delivers 45 A at a terminal voltage of 220 V. The armature and the shunt field resistances are 0.01Ω and 44Ω respectively. The stray losses are 375 W. The percentage efficiency of the DC generator is _____

S1 Correct answer is 86.84%.

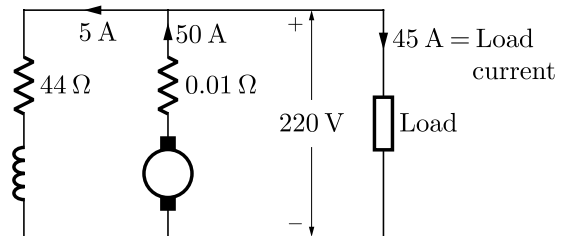

$$\begin{aligned}
 \text{Total copper losses} &= 5^2 \times 44 + 50^2 \times 0.01 \\
 &= 1100 + 25 \\
 &= 1125 \text{ W}
 \end{aligned}$$

other losses (given as stray losses) = 375 W

$$\text{Total losses} = 1500 \text{ W}$$


$$\text{Output} = 220 \times 45 = 9900 \text{ W}$$

$$\text{Efficiency} = \frac{9900}{11400} = 86.84\%$$

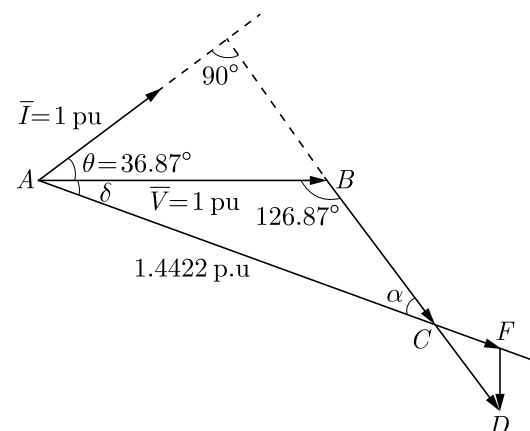Q58 A three-phase, 50 Hz salient-pole synchronous motor has a per-phase direct-axis reactance (X_d) of 0.8 pu and a per phase quadrature-axis reactance (X_q) of 0.6 pu. resistance of the machine is negligible. It is drawing full-load current at 0.8 pf (leading). When the terminal voltage is 1 pu, per-phase induced voltage, in pu, is _____

S1 Correct answer is 1.6086 p.u.

Phasor diagram for E is constructed as below.



$$\begin{aligned}
 AC^2 &= AB^2 + BC^2 - 2(AB)(BC) \cos 126.87^\circ \\
 &= 1 + 0.36 + 1.2(0.6) \\
 &= 2.08
 \end{aligned}$$

$$\begin{aligned}
 AC &= \sqrt{2.08} \\
 &= 1.4422
 \end{aligned}$$

$$\frac{1.4422}{0.8} = \frac{1}{\sin \alpha}$$

$$\alpha = 33.7^\circ, \cos \alpha = 0.832$$


$$CF = 0.1664$$

$$AF = E = 1.6086 \text{ p.u}$$

Q59 A single-phase 22 kVA, 2200 V/220, 50 Hz, distribution transformer is to be connected as an auto transformer to get an output voltage of 2420 V. Its maximum kVA rating as an auto-transformer is

- (A) 22
- (B) 24.2
- (C) 242
- (D) 2420

S1 Correct option is (C).

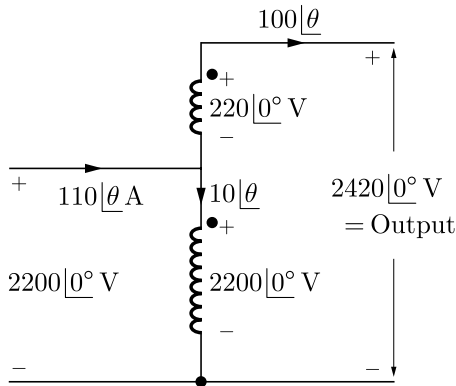

$$\text{Rated } l_v \text{ current} = \frac{22000}{220} = 100 \text{ A}$$

$$\begin{aligned} \text{Maximum kVA rating} &= \frac{2200 \times 110}{1000} \\ &= \frac{2420 \times 100}{1000} \\ &= 242 \text{ kVA} \end{aligned}$$

Q60 A single-phase full-bridge voltage source inverter (VSI) is fed from a 300 V battery. A pulse of 120° duration is used trigger the appropriate device in each half cycle. The rms value of the fundamental component of the output voltage, in volts, is



- (A) 234
- (B) 245
- (C) 300
- (D) 331

S1 Correct option is (A).

$$\begin{aligned} \text{Pulse width } 2d &= 120^\circ \\ V_{01} &= \frac{2\sqrt{2}}{\pi} V_{dc} \sin d \\ &= 0.9 \times 300 \times \sin 60^\circ \\ &= 233.8 \text{ V} \end{aligned}$$


Q61 A single-phase transmission line has two conductors each of 10 mm radius. These are fixed at a center-to-center distance of 1 m in a horizontal plane. This is now converted to a three-phase transmission line by introducing a third conductor of the same radius. This conductor is fixed at an equal distance D from the two single-phase conductors. The three-phase line is fully transposed. The positive sequence inductance per phase of the three phase system is to be 5% more than that of the inductance per conductor of the single phase system. The distance D , in meters, is _____

S1 Correct answer is 1.438.

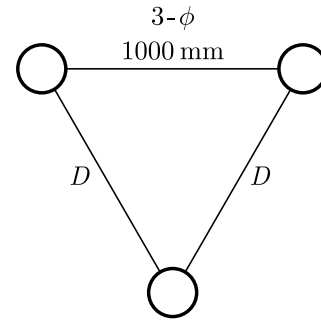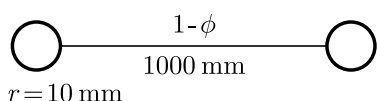


$$\begin{aligned} 1.05 \times L_{1-\phi} &= L_{3\phi} \\ 1.05 \times 0.2 \ln \frac{1000}{0.788 \times 100} &= 0.2 \ln \frac{(1000D^2)^{\frac{1}{3}}}{0.788 \times 10} \\ \left(\frac{1000}{7.88}\right)^{1.05} &= \frac{(1000D^2)^{\frac{1}{3}}}{7.88} \\ D &= 1438 \text{ mm} = 1.438 \text{ m} \end{aligned}$$

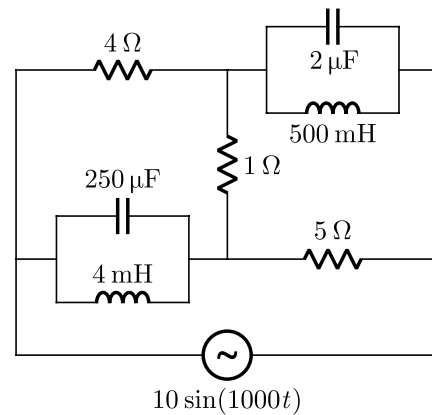Q62 In the circuit shown below, the supply voltage is $10 \sin(1000t)$ volts. The peak value of the steady state current through the 1Ω resistor, in amperes, is _____



S1 Correct answer is 1.

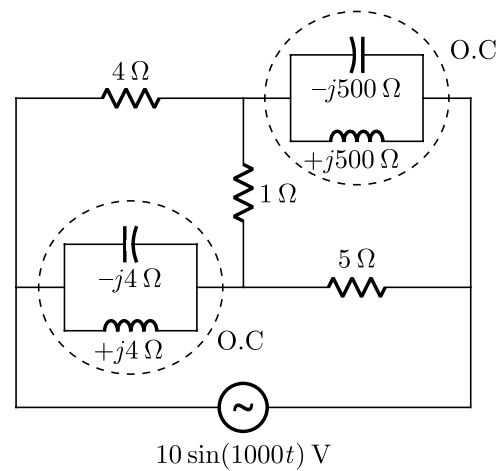

$$\begin{aligned} I_{1\Omega} &= \frac{V}{4 + 1 + 5} = \frac{10 \sin 1000t}{10} \\ I_{1\Omega} &= 1 \sin 1000t \text{ A} \end{aligned}$$

The peak value of the steady state current through 1Ω register is 1 A.

Q63 A dc voltage with ripple is given by $v(t) = [100 + 10 \sin(\omega t) - 5 \sin(3\omega t)]$ volts. Measurements of this voltage $v(t)$, made by moving-coil and moving iron voltmeters, show readings of V_1 and V_2 respectively. The value of $V_2 - V_1$, in volts, is _____

S1 Correct answer is 0.31 V.

PMMC; $V_1 = 100$ V


M.I; $V_2 = \sqrt{(100)^2 + \left(\frac{10}{\sqrt{2}}\right)^2 + \left(\frac{5}{\sqrt{2}}\right)^2}$

$$= \sqrt{10000 + 50 + 12.5}$$

$$= 100.31$$

$$V_2 - V_1 = 0.31$$

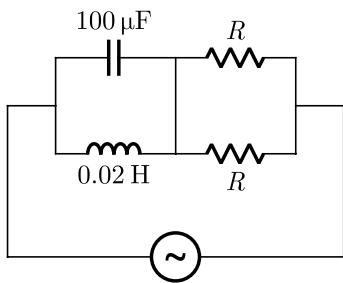
Q64 The circuit below is excited by a sinusoidal source. The value of R , in Ω for which the admittance of the circuit becomes a pure conductance at all frequencies is




S1 Correct answer is 14.14.

$$R = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.02}{100\mu}} = \sqrt{200} = 14.14 \Omega$$

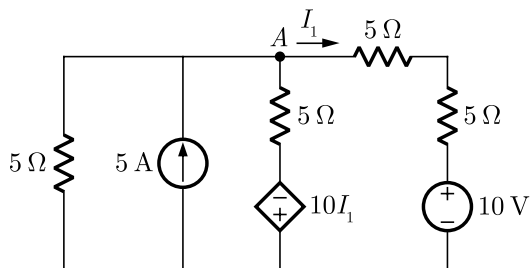Q65 In the circuit shown below, the node voltage V_A is ----- V.



S1 Correct answer is 11.42.

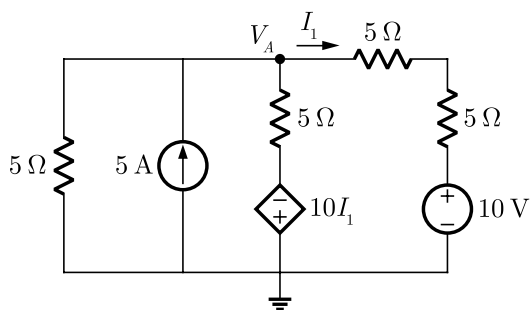

$$\frac{V_A}{5} - 5 + \frac{(V_A + 10I_1)}{5} + \frac{(V_A - 10)}{10} = 0$$

$$2V_A - 50 + 2V_A + 20I_1 + V_A - 10 = 0$$

$$5V_A + 20I_1 = 60 \quad \dots(1)$$

$$I_1 = \frac{(V_A - 10)}{10} \quad \dots(2)$$

So, $5V_A + 20\left[\frac{V_A - 10}{10}\right] = 60$
 $7V_A = 80 \rightarrow V_A = \frac{80}{7}$
 $V_A = 11.42$ Volts